 


Task 1: Positive Edge Triggered D Flip-Flop

A positive edge triggered D flip-flop is a clock synchronous sequential circuit that holds onto the previous input and reads for new inputs only on positive edges on the clock. It uses two D latches and 2 inverters to achieve this.

D	CLK	Q	QN
0	↑	0	1
1	↑	1	0
X	0	Last Q	Last QN
X	1	Last Q	Last QN




```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  library UNISIM;
4  use UNISIM.VComponents.all;
5
6  entity pet_d_ff is
7      Port ( CLK : in  STD_LOGIC;
8            D : in  STD_LOGIC;
9            Q : out  STD_LOGIC;
10           QN : out  STD_LOGIC);
11 end pet_d_ff;
12
13 architecture Behavioral of pet_d_ff is
14     signal CLK_L,Q1,Q2: std_logic;
15     component LD
16         generic(INIT: bit := '0');
17         port(D,G: in std_logic;
18             Q: out std_logic);
19     end component;
20     component INV port(I: in std_logic; O: out std_logic); end component;
21 begin
22     U0: INV port map(CLK,CLK_L);
23     U1: LD port map(D,CLK_L,Q1);
24     U2: LD port map(Q1,CLK,Q2);
25     U3: Q <= Q2;
26     U4: INV port map(Q2,QN);
27 end Behavioral;
```

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY TB_pet_d_ff IS
5  END TB_pet_d_ff;
6
7  ARCHITECTURE behavior OF TB_pet_d_ff IS
8      COMPONENT pet_d_ff
9      PORT(
10         CLK : IN  std_logic;
11         D : IN  std_logic;
12         Q : OUT  std_logic;
13         QN : OUT  std_logic
14     );
15     END COMPONENT;
16
17     --Inputs
18     signal CLK : std_logic := '0';
19     signal D : std_logic := '0';
20     --Outputs
21     signal Q : std_logic;
22     signal QN : std_logic;
23
24     -- Clock period definitions
25     constant CLK_period : time := 10 ns;
26
```


```

26
27 BEGIN
28     -- Instantiate the Unit Under Test (UUT)
29     uut: pet_d_ff PORT MAP (
30         CLK => CLK,
31         D => D,
32         Q => Q,
33         QN => QN
34     );
35
36     -- Clock process definitions
37     CLK_process :process
38     begin
39         CLK <= '0';
40         wait for CLK_period/2;
41         CLK <= '1';
42         wait for CLK_period/2;
43     end process;
44
45     -- Stimulus process
46     stim_proc: process
47     begin
48         wait for 20 ns;
49         d <= '0';
50         wait for CLK_period*2;
51         d <= '1';
52         wait for CLK_period*2;
53         d <= '0';
54         wait for CLK_period*2;
55         d <= '1';
56         wait for CLK_period*2;
57         wait;
58     end process;
59 END;


```

 

 
This outcome is correct because D is 0 right before the clock tick therefore Q should be 0 and QN should be 1.



 
This outcome is correct because D is 0 right before the clock tick therefore Q should be 0 and QN should be 1.



 
This outcome is correct because D is 0 right before the clock tick therefore Q should be 0 and QN should be 1.



 
This outcome is correct because D is 1 right before the clock tick therefore Q should be 1 and QN should be 0.



 
This outcome is correct because D is 1 right before the clock tick therefore Q should be 1 and QN should be 0.



 This outcome is correct because D is 0 right before the clock tick therefore Q should be 0 and QN should be 1.



 
This outcome is correct because D is 0 right before the clock tick therefore Q should be 0 and QN should be 1.



This outcome is correct because D is 1 right before the clock tick therefore Q should be 1 and QN should be 0.

 Task 2: T Flip-Flop

A T flip-flop is a clock synchronous sequential circuit that flips the value of Q and QN at each clock tick. It uses a positive edge triggered D flip-flop to achieve this.




```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 library UNISIM;
4 use UNISIM.VComponents.all;
5
6 entity t_ff is
7     Port ( CLK : in  STD_LOGIC;
8           Q : out  STD_LOGIC;
9           QN : out  STD_LOGIC);
10 end t_ff;
11
12 architecture Behavioral of t_ff is
13     component pet_d_ff port(CLK: in std_logic;
14                             D: in std_logic;
15                             Q: out std_logic;
16                             QN: out std_logic);
17     end component;
18     signal Q1,Q1_L: std_logic;
19 begin
20     U0: pet_d_ff port map(CLK,Q1_L,Q1,Q1_L);
21     U1: Q <= Q1;
22     U2: QN <= Q1_L;
23 end Behavioral;
```

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4
5  ENTITY TB_t_ff IS
6  END TB_t_ff;
7
8  ARCHITECTURE behavior OF TB_t_ff IS
9      COMPONENT t_ff
10     PORT(
11         CLK : IN  std_logic;
12         Q : OUT  std_logic;
13         QN : OUT  std_logic
14     );
15     END COMPONENT;
16
17     --Inputs
18     signal CLK : std_logic := '0';
19     --Outputs
20     signal Q : std_logic;
21     signal QN : std_logic;
22
23     -- Clock period definitions
24     constant CLK_period : time := 10 ns;
25
26
27 BEGIN
28     uut: t_ff PORT MAP (
29         CLK => CLK,
30         Q => Q,
31         QN => QN
32     );
33
34     -- Clock process definitions
35     CLK_process :process
36     begin
37         CLK <= '0';
38         wait for CLK_period/2;
39         CLK <= '1';
40         wait for CLK_period/2;
41     end process;
42 END;

```

 This outcome is correct because it can be seen that at each clock tick, the values of Q and QN flip.

Task 3: 4-bit Binary Ripple Counter

A 4-bit ripple counter is a series of 4 T flip-flops that count the number of clock tick that have passed and then stays asserted for that many clock ticks. The n-th T flip-flop will stay negated for 2^n clock ticks then switch to being asserted for 2^n clock ticks. For example, the first T flip-flop will flip every clock tick, the second T flip-flop will switch every two clock tick, and so on.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  library UNISIM;
4  use UNISIM.VComponents.all;
5
6  entity ripple_counter is
7      Port ( CLK : in  STD_LOGIC;
8            Q0  : out  STD_LOGIC;
9            Q1  : out  STD_LOGIC;
10           Q2  : out  STD_LOGIC;
11           Q3  : out  STD_LOGIC);
12 end ripple_counter;
13
14 architecture Behavioral of ripple_counter is
15     component t_ff port(CLK: in std_logic;
16                        Q: out std_logic;
17                        QN: out std_logic);
18     end component;
19     signal Q0_L,Q1_L,Q2_L,Q3_L: std_logic;
20 begin
21     U0: t_ff port map(CLK,Q0,Q0_L);
22     U1: t_ff port map(Q0_L,Q1,Q1_L);
23     U2: t_ff port map(Q1_L,Q2,Q2_L);
24     U3: t_ff port map(Q2_L,Q3,Q3_L);
25 end Behavioral;
26
27


```

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY TB_ripple_counter IS
5  END TB_ripple_counter;
6
7  ARCHITECTURE behavior OF TB_ripple_counter IS
8      COMPONENT ripple_counter
9      PORT(
10         CLK : IN    std_logic;
11         Q0  : OUT   std_logic;
12         Q1  : OUT   std_logic;
13         Q2  : OUT   std_logic;
14         Q3  : OUT   std_logic
15     );
16     END COMPONENT;
17
18     --Inputs
19     signal CLK : std_logic := '0';
20     --Outputs
21     signal Q0 : std_logic;
22     signal Q1 : std_logic;
23     signal Q2 : std_logic;
24     signal Q3 : std_logic;
25
26     -- Clock period definitions
27     constant CLK_period : time := 10 ns;
28
```

```

28
29 BEGIN
30     uut: ripple_counter PORT MAP (
31         CLK => CLK,
32         Q0 => Q0,
33         Q1 => Q1,
34         Q2 => Q2,
35         Q3 => Q3
36     );
37
38     -- Clock process definitions
39     CLK_process :process
40     begin
41         CLK <= '0';
42         wait for CLK_period/2;
43         CLK <= '1';
44         wait for CLK_period/2;
45     end process;
46 END;
47

```

 

This outcome is correct because Q0 flips every clock tick, Q1 flips every two clock ticks, Q2 flips every four clock ticks, and Q4 flips every eight clock ticks.