 


Task 1: S'-R' Latch

A S'-R' latch is a type of sequential circuit that uses two NAND gates in a feedback loop to create a circuit that can hold on to a signal it has previously gotten. It takes two inputs S_L and R_L and outputs Q and QN based on the following truth table:

S_L	R_L	Q	QN
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Last Q	Last QN




```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  library UNISIM;
4  use UNISIM.VComponents.all;
5
6  entity srlatch is
7      Port (R_L: in std_logic;
8            S_L: in std_logic;
9            Q: out std_logic;
10           QN: out std_logic);
11 end srlatch;
12
13 architecture Behavioral of srlatch is
14     signal tmp1,tmp2: std_logic;
15     component NAND2 port (I1,I0: in std_logic;
16                           O: out std_logic);
17     end component;
18 begin
19     U0: NAND2 port map (S_L,tmp2,tmp1);
20     U1: NAND2 port map (R_L,tmp1,tmp2);
21     Q <= tmp1;
22     QN <= tmp2;
23 end Behavioral;
```


```

1  library ieee;
2  use ieee.std_logic_1164.ALL;
3
4  entity testbench is
5  end testbench;
6
7  architecture behavior of testbench is
8      --Component Declaration
9      component srlatch
10     port(R_L: in std_logic;
11          S_L: in std_logic;
12          Q: out std_logic;
13          QN: out std_logic);
14     end component;
15
16     --Inputs
17     signal R_L:  std_logic := '0';
18     signal S_L :  std_logic := '0';
19
20     --Outputs
21     signal Q: std_logic;
22     signal QN: std_logic;
23 begin
24     uut: srlatch port map(R_L => R_L,
25                          S_L => S_L,
26                          Q => Q,
27                          QN => QN);
28
29     stim_proc: process
30     begin
31         s_l <= '0'; r_l <= '0'; wait for 50 ns;
32         s_l <= '0'; r_l <= '1'; wait for 50 ns;
33         s_l <= '1'; r_l <= '1'; wait for 50 ns;
34         s_l <= '1'; r_l <= '0'; wait for 50 ns;
35         s_l <= '1'; r_l <= '1'; wait for 50 ns;
36         s_l <= '0'; r_l <= '0'; wait for 50 ns;
37         wait;
38     end process;
39 end;


```

 

 
This outcome is correct because both S_L and R_L are negated, therefore Q and QN should be asserted which can be seen above.



 
This outcome is correct because S_L is negated and R_L is asserted, therefore Q should be asserted and QN should be negated which can be seen above.



 
This outcome is correct because both S_L and R_L are asserted, therefore Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 This outcome is correct because S_L is asserted and R_L is negated, therefore Q should be negated and Q_N should be asserted which can be seen above.



 This outcome is correct because both S_L and R_L are asserted, therefore Q and Q_N should be the last values it had which in this case it is Q being negated and Q_N being asserted. This can be seen above.




This outcome is correct because both S_L and R_L are negated, therefore Q and Q_N should be asserted which can be seen above.

Task 2: S-R Latch with Enable

A S-R latch with enable is a type of sequential circuit that uses a $S'-R'$ latch and two NAND gates to create a $S'-R'$ latch that can be enabled and disabled using the enable input. It takes three inputs S , R , and C and outputs Q and Q_N based on the following truth table:

S	R	C	Q	QN
0	0	1	Last Q	Last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
X	X	0	Last Q	Last QN

 

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 library UNISIM;
4 use UNISIM.VComponents.all;
5
6 entity srlatchen is
7     port (S: in std_logic;
8           R: in std_logic;
9           C: in std_logic;
10          Q: out std_logic;
11          QN: out std_logic);
12 end srlatchen;
13
14 architecture Behavioral of srlatchen is
15     signal tmp1,tmp2: std_logic;
16     component NAND2 port (I1,I0: in std_logic; O: out std_logic);
17     end component;
18     component srlatch port (R_L,S_L: in std_logic; Q,QN: out std_logic);
19     end component;
20 begin
21     U0: NAND2 port map (S,C,tmp1);
22     U1: NAND2 port map (R,C,tmp2);
23     U2: srlatch port map (tmp2,tmp1,Q,QN);
24 end Behavioral;
25
```


```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  entity testbench is
5  end testbench;
6
7  architecture Behavior of testbench is
8      --Component Declaration
9      component srlatchen port(S: in std_logic;
10                             R: in std_logic;
11                             C: in std_logic;
12                             Q: out std_logic;
13                             QN: out std_logic);
14  end component;
15
16      --Inputs
17      signal S: std_logic := '0';
18      signal R: std_logic := '0';
19      signal C: std_logic := '0';
20
21      --Outputs
22      signal Q: std_logic;
23      signal QN: std_logic;
24  begin
25      uut: srlatchen port map(S => S,
26                             R => R,
27                             C => C,
28                             Q => Q,
29                             QN => QN);
30
```




```

31 stim_proc: process
32 begin
33     --c is asserted
34     s <= '0'; r <= '1'; c <= '1'; wait for 50 ns;
35     s <= '0'; r <= '0'; c <= '1'; wait for 50 ns;
36     s <= '1'; r <= '0'; c <= '1'; wait for 50 ns;
37     s <= '0'; r <= '0'; c <= '1'; wait for 50 ns;
38
39     --c is negated
40     s <= '0'; r <= '1'; c <= '0'; wait for 50 ns;
41     s <= '0'; r <= '0'; c <= '0'; wait for 50 ns;
42     s <= '1'; r <= '0'; c <= '0'; wait for 50 ns;
43     s <= '0'; r <= '0'; c <= '0'; wait for 50 ns;
44     s <= '1'; r <= '1'; c <= '0'; wait for 50 ns;
45
46     --c is again asserted
47     s <= '1'; r <= '1'; c <= '1'; wait for 50 ns;
48
49     wait;
50 end process;
51 end;


```

 

 
This outcome is correct because S is negated and both R and C are asserted, therefore Q should be negated and QN should be asserted which can be seen above.



 
This outcome is correct because both S and R is negated and C is asserted, therefore Q and QN should be the last values it had which in this case it is Q being negated and QN being asserted. This can be seen above.



 
This outcome is correct because both S and C are asserted and R is negated, therefore Q should be asserted and QN should be negated which can be seen above.



 
This outcome is correct because both S and R is negated and C is asserted, therefore Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 
This outcome is correct because C is negated, therefore the values of S and R should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 
This outcome is correct because C is negated, therefore the values of S and R should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 
This outcome is correct because C is negated, therefore the values of S and R should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 This outcome is correct because C is negated, therefore the values of S and R should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 This outcome is correct because C is negated, therefore the values of S and R should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.




This outcome is correct because S, R, and C are all asserted, therefore Q should be asserted and QN should be asserted which can be seen above.

Task 1: D Latch

A D latch is a type of sequential circuit that uses a S-R latch with enable and an inverter to create a D latch that can be used like the S-R latch with enable but has less states allowing for fewer points of failure. It takes two inputs D and C and outputs Q and QN based on the following truth table:

C	D	Q	QN
1	0	0	1
1	1	1	0
0	X	Last Q	Last QN

D Latch

 

```


1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  library UNISIM;
4  use UNISIM.VComponents.all;
5
6  entity dlatch is
7      port(C: in std_logic;
8           D: in std_logic;
9           Q: out std_logic;
10          QN: out std_logic);
11 end dlatch;
12
13 architecture Behavioral of dlatch is
14     signal D_L: std_logic;
15     component INV port (I: in std_logic; O: out std_logic);
16     end component;
17     component srlatchen port (S,R,C: in std_logic; Q,QN: out std_logic);
18     end component;
19 begin
20     U0: INV port map(D,D_L);
21     U1: srlatchen port map(D,D_L,C,Q,QN);
22 end Behavioral;
23

```


```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  entity testbench is
5  end testbench;
6
7  architecture behavior of testbench is
8      --Component Declaration
9      component dlatch port(
10         C : in  std_logic;
11         D : in  std_logic;
12         Q : out std_logic;
13         QN : out std_logic);
14     end component;
15
16     --Inputs
17     signal C : std_logic := '0';
18     signal D : std_logic := '0';
19
20     --Outputs
21     signal Q : std_logic;
22     signal QN : std_logic;
23 begin
24     uut: dlatch port map(C => C,
25                          D => D,
26                          Q => Q,
27                          QN => QN);
28
29     stim_proc: process
30     begin
31         d <= '0'; c <= '1'; wait for 50 ns;
32         d <= '1'; c <= '1'; wait for 50 ns;
33         d <= '0'; c <= '0'; wait for 50 ns;
34         d <= '1'; c <= '0'; wait for 50 ns;
35         d <= '0'; c <= '1'; wait for 50 ns;
36         d <= '1'; c <= '1'; wait for 50 ns;
37         wait;
38     end process;
39 end;


```

 

 
This outcome is correct because C is asserted and D is negated, therefore Q should be negated and QN should be asserted which can be seen above.



 
This outcome is correct because both C and D are asserted, therefore Q should be asserted and QN should be negated which can be seen above.



 
This outcome is correct because C is negated, therefore the value D should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 This outcome is correct because C is negated, therefore the value D should be ignored and Q and QN should be the last values it had which in this case it is Q being asserted and QN being negated. This can be seen above.



 This outcome is correct because C is asserted and D is negated, therefore Q should be negated and QN should be asserted which can be seen above.



This outcome is correct because both C and D are asserted, therefore Q should be asserted and QN should be negated which can be seen above.